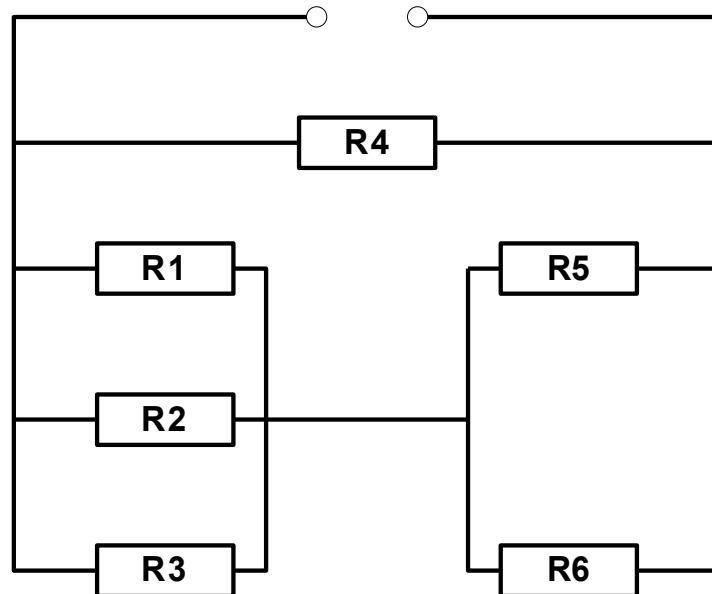


**Aufgabe 1:** Berechne  $R_4$ !



$$R_0 = 0,25 \text{ k}\Omega, R_1 = 20 \Omega, R_2 = 20 \text{ k}\Omega, R_3 = 40 \Omega, R_5 = 800 \Omega, R_6 = 1000 \Omega$$


$$\frac{1}{R_{123}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{20 \Omega} + \frac{1}{20.000 \Omega} + \frac{1}{40 \Omega} = \frac{1501}{20000 \Omega} \Leftrightarrow R_{123} = \frac{20.000 \Omega}{1501} \approx 13,32 \Omega$$

$$\frac{1}{R_{56}} = \frac{1}{R_5} + \frac{1}{R_6} = \frac{1}{800 \Omega} + \frac{1}{1.000 \Omega} = \frac{9}{4000 \Omega} \Leftrightarrow R_{56} = \frac{4.000 \Omega}{9} \approx 444,44 \Omega$$

$$R_{12356} = R_{123} + R_{56} = 457,76 \Omega$$

$$\frac{1}{R_{Ges}} = \frac{1}{R_{12356}} + \frac{1}{R_4} \Leftrightarrow \frac{1}{R_4} = \frac{1}{R_{Ges}} - \frac{1}{R_{12356}} = \frac{1}{250 \Omega} - \frac{1}{457,76 \Omega} = \frac{1}{550,83 \Omega} \Leftrightarrow R_{Ges} = 550,83 \Omega$$

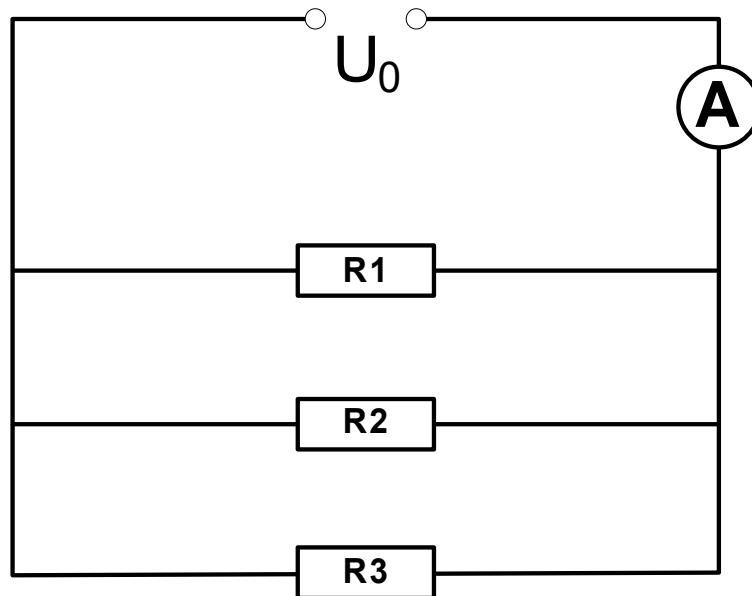**Aufgabe 2:** Berechne  $R_1$  und  $R_2$ ! (Der Innenwiderstand des Messgerätes wird vernachlässigt.)



$U_0 = 60 \text{ V}$ ,  $I_0 = 0,2 \text{ A}$ ,  $R_3 = 0,6 \text{ k}\Omega$ ,  $R_1$  ist doppelt so groß wie  $R_2$

$$R_{Ges} = \frac{U_0}{I_0} = \frac{60 \text{ V}}{0,2 \text{ A}} = 300 \Omega \quad R_1 = 2 R_2$$

$$\frac{1}{R_{Ges}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{2R_2} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{3}{2R_2} + \frac{1}{R_3}$$

$$\Leftrightarrow \frac{3}{2} R_2 = \frac{1}{R_{Ges}} - \frac{1}{R_3} = \frac{1}{300 \Omega} - \frac{1}{600 \Omega} = \frac{1}{600 \Omega} \quad \Leftrightarrow \frac{1}{R_2} = \frac{2}{3 \cdot 600 \Omega} = \frac{2}{1800 \Omega}$$

$$\Leftrightarrow R_2 = 900 \Omega \quad \Rightarrow R_1 = 1800 \Omega$$